

Notes on PA Design

Memory effect

- Electrical → non-constant distortion behavior at different modulation frequencies (tone spacing) is called as electrical memory.
- Thermal → Low freq envelope of signal heats up substrate and affects wafer/transistor properties for incoming signal.

↳ Trapping effect → (related to semiconductor)


Electrical Memory

- IM3 are produced through
 - 3rd order distortion ($3a^2b, 3ab^2$)
 - 2nd order interaction
 - Beat ($\omega_2 - \omega_1$ with $2\omega_1/2\omega_2$)
 - 2nd harmonic ($2\omega_1/2\omega_2$ with ω_1/ω_2)

- An amplifier has many internal nodes which can generate higher order terms. ∴ it is not sufficient to model through one polynomial from input to output.


For example, BJT r_{π} is one poly and r_o is one polynomial. Overall you can say response is cascade of two polys which will have 3 major sources of IM3 as mentioned above.

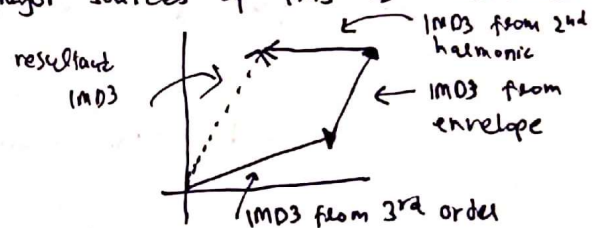→ Usually 2nd harm IM3 has 180° phase because $2\omega_1 - \omega_2$ / $2\omega_2 - \omega_1$ of this negative signs. (negative of two tones) needed to generate IM3




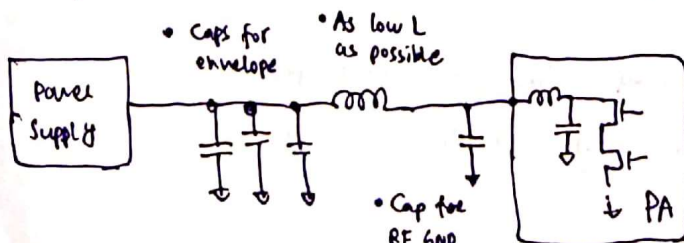- Problem is not that there are additional IM3 sources. Problem is that 2nd harmonic or beat impedance behavior with frequency is poorly controlled. ∴ different tone spacings don't generate different same magnitude of IM3s.
- Non-linearities can be considered as current sources, and voltage they produce depend on node impedances.
- Memory effect is solved to the first order by providing fixed impedance. However, that is still an issue for beat/envelope because that current has to come from relatively remote power supply as you cannot provide big enough cap for kHz-MHz envelopes to provide current. Therefore, there are inductances and resistances which create voltage drop depending on envelope variation. ∴ V_{DD} that PA gets is not constant and has ripples which produces IM3s. ∴

→ Goal is to provide fixed and very low impedance




Bias network impedance Response

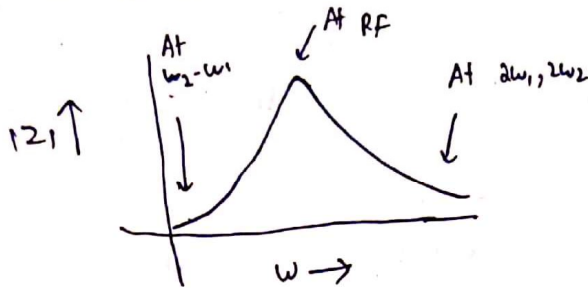


• This is how we should optimize bias network impedance.

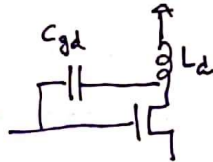⇒ low impedance at $\omega_2 - \omega_1$ requires use of small series inductors which create stability issues by presenting negative resistance at input.



→ C_{gd} transfeers L_d to negative R. Y_{in} from $C_{gd} \approx C_{gd}(1+A) \approx j\omega C(1+g_m j\omega L)$
 $\approx -\omega^2 g_m C_{gd} L_d$

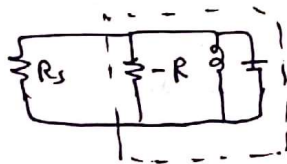→ low freq, small $-R$ in shunt → more dangerous



→ will oscillate if $R_s < R$


$$\therefore \frac{-R_s R}{R_s - R} \rightarrow \text{ive if } R_s > R$$

⇒ Shaping 2nd harmonic may be desirable / undesirable depending upon waveform engineering.

Why memory effect is bad?

→ c2 it may create asymmetric IM3 responses
 → distortion depends on signal BW ∴ varies signal to signal

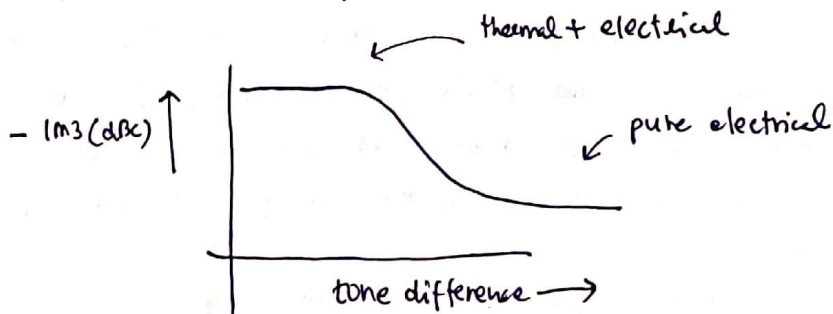• Because memory-less predistortion becomes ineffective



• At high f, wafer does not get sufficient time to heat up.

∴ thermal memory effect is visible at low f. only.